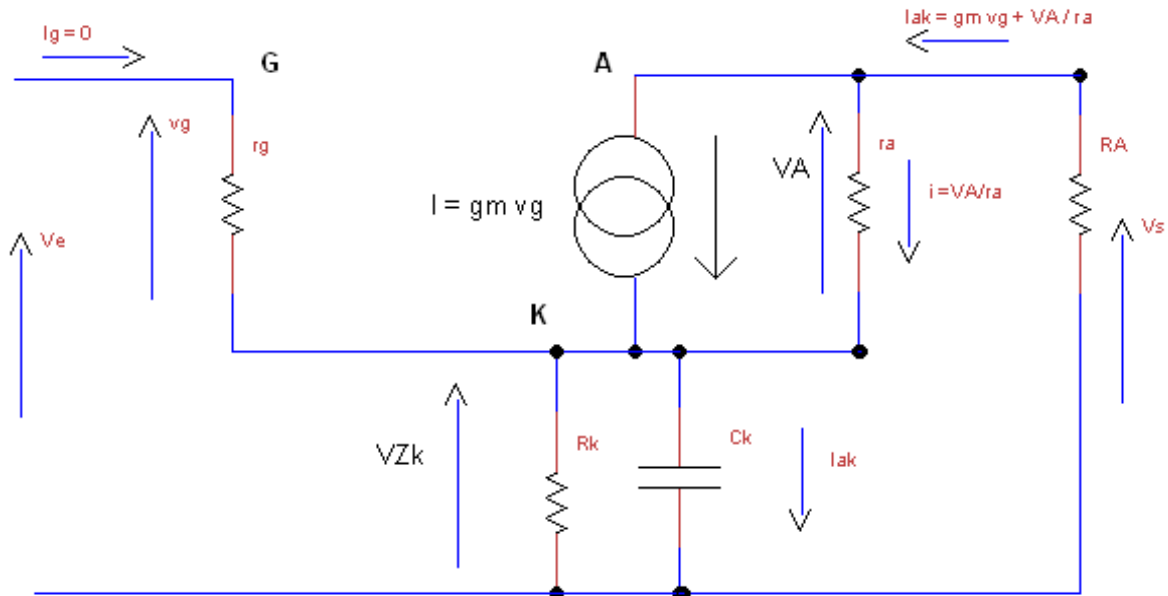


Common cathode triode amplifier

Low cut-off frequency

common cathode amp stage with partially bypassed cathode



With :

- r_a = internal resistance of the triode (cf Datasheet)
- V_A = anode – cathode voltage
- g_m = transconductance (cf Datasheet)
- Z_k = complex impedance on the cathode ($R_k // C_k$ – with C_k being a NOT perfect capacitance)
- R_A load impedance on the anode
- r_g = grid resistance held as infinite

The gain of the stage is :

$$A_v = \frac{V_s}{V_e} = \frac{-\mu R_A}{R_A + r_a + (\mu + 1) Z_k} \quad (1)$$

This formula helps computing precisely the low cut-off frequency induced by the bypass capacitor C_k

In the bandwidth $Z_k = 0$ and the gain is $A_v = \frac{-\mu R_A}{R_A + r_a}$.

In fact $Z_k = R_k // C_k = \frac{R_k}{1 + j\omega C_k R_k}$

We see that for $\omega = \infty$ $Z_k = 0$ and the gain is maximum. The cut-off frequency is confirmed as a low frequency and the problem becomes how low the value of ω can be before the gain reaches the value of $A_v - 3 \text{ dB}$?

In fact for a same value of V_e (V_{in}) we will reach the low limit of the bandwidth when V_s (V_{out}) will be diminished by 3 dB, therefore at the cut-off $V_{sc} = \frac{V_s}{\sqrt{2}}$.

For this it is sufficient that the magnitude of the denominator of (1) equals $\sqrt{2}(R_A + r_a)$.

At the cut-off frequency ω we have :

$$\sqrt{2}(R_A + r_a) = \left| R_A + r_a + (\mu + 1) \frac{R_k}{1 + j\omega C_k R_k} \right|$$

$$\sqrt{2} = \frac{\left| R_A + r_a + (\mu + 1) \frac{R_k}{1 + j\omega C_k R_k} \right|}{\left| R_A + r_a \right|}$$

multiplied high and low by $1 + j\omega C_k R_k$ it yields :

$$\sqrt{2} = \frac{\left| (R_A + r_a)(1 + j\omega C_k R_k) + (\mu + 1)R_k \right|}{\left| (R_A + r_a)(1 + j\omega C_k R_k) \right|}$$

$$\sqrt{2} = \frac{\left| (R_A + r_a) + (\mu + 1)R_k + j(R_A + r_a)R_k C_k \omega \right|}{\left| R_A + r_a + j(R_A + r_a)R_k C_k \omega \right|}$$

Hence simplified by $R_A + r_a$:

$$\sqrt{2} = \frac{\left| 1 + \frac{(\mu + 1) Rk}{Ra + ra} + jRkCk \omega_0 \right|}{\left| 1 + jRkCk \omega_0 \right|}$$

Dividing the magnitudes yields :

$$\sqrt{2} = \frac{\sqrt{\left(1 + \frac{(\mu + 1) Rk}{Ra + ra} \right)^2 + Rk^2 Ck^2 \omega_0^2}}{\sqrt{1 + Rk^2 Ck^2 \omega_0^2}}$$

Squaring it all :

$$2 + 2 Rk^2 Ck^2 \omega_0^2 = \left(1 + \frac{(\mu + 1) Rk}{Ra + ra} \right)^2 + Rk^2 Ck^2 \omega_0^2$$

$$2 + Rk^2 Ck^2 \omega_0^2 = \left(1 + \frac{(\mu + 1) Rk}{Ra + ra} \right)^2$$

$$\omega_0^2 = \frac{\left(1 + \frac{(\mu + 1) Rk}{Ra + ra} \right)^2 - 2}{Rk^2 Ck^2}$$

With $\omega_0 = 2 \pi f$ (Hz)

$$f_{(Hz)} = \frac{1}{2 \pi Rk Ck} \sqrt{\left[1 + \frac{(\mu + 1) Rk}{RA + ra} \right]^2 - 2}$$

Of course if f is given , the value of the capacitance Ck can be found with the same formula, just reversing both.